



## DIGITAL DESIGN & COMPUTER ORGANISATION

### FINITE STATE MACHINES

**Sudarshan T S B., Ph.D.**

Department of Computer Science & Engineering

1

1



## DIGITAL DESIGN & COMPUTER ORGANISATION

### FINITE STATE MACHINES

**Sudarshan T S B., Ph.D.**

Department of Computer Science & Engineering

2

2

## FINITE STATE MACHINES

## Course Outline



- Digital Design
  - ▶ Combinational logic design
  - ▶ Sequential logic design
    - ★ Finite State Machines
- Computer Organization
  - ▶ Architecture (microprocessor instruction set)
  - ▶ Microarchitecture (microprocessor operation)

## Concepts covered

- Finite State Machines
  - ▶ Mealy and Moore Machines

24/09/21

Sudarshan TSB, PES University

3

3

## FINITE STATE MACHINES

## Example-2




- Express State Equation
- Construct a State Table
- Construct a State Diagram

**State Equation:**

$$A(t+1) = AX + BX$$

$$B(t+1) = A'X$$

$$Y = X' (A + B)$$

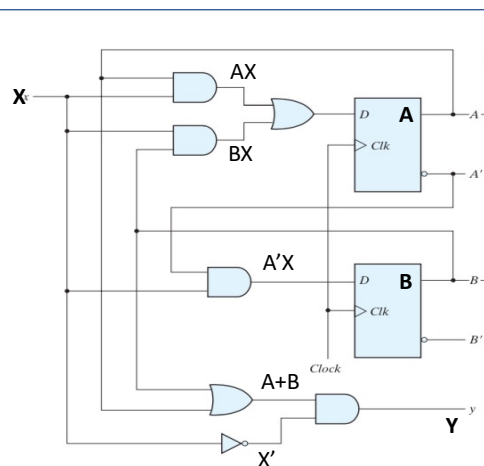

24/09/21


Sudarshan TSB, PES University

4

4

# FINITE STATE MACHINES

### Example-2 (contd)

 

24/09/21

Sudarshan TSB, PES University

5

5

## FINITE STATE MACHINES

### Example-3

- Design a circuit using State Transition Diagram that has a serial input X and an output Z.
- Z should be 1 coinciding with the last bit of the pattern **010** or else Z is 0.
- Construct a Mealy machine and Moore machine for both **non-overlapping pattern** detection and **overlapping pattern** detection

24/09/21

Sudarshan TSB, PES University

6


6

## FINITE STATE MACHINES
 
## Example-3 (contd)

Mealy Non-Overlapping:

$2/p: X \quad \overline{010} \overline{1010}$   
 $o/p: Z \quad 0010001$



24/09/21

Sudarshan TSB, PES University

7

7

## FINITE STATE MACHINES

## Example-3 (contd)

Moore Overlapping:

24/09/21

Sudarshan TSB, PES University

8

8


## FINITE STATE MACHINES
 
## Example- 4




- Traffic light controller

- ▶ Traffic sensors:  $T_A, T_B$  (TRUE when there's traffic)
- ▶ Lights:  $L_A, L_B$



*CLK with 5-sec period*  
*Reset to control the initial state*

 - Inputs:  $CLK, Reset, T_A, T_B$
- Outputs:  $L_A, L_B$



24/09/21

Sudarshan TSB, PES University

9


9

## FINITE STATE MACHINES

## Example-4 (contd)

 **FSM Diagram:**

- Moore FSM: outputs labeled in each state



24/09/21

Sudarshan TSB, PES University

10


10

## FINITE STATE MACHINES

## Example-4 (contd)

**FSM Diagram:**

- Moore FSM

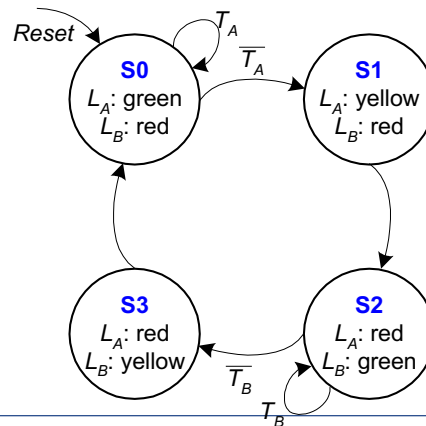

24/09/21

Sudarshan TSB, PES University

11

11


## FINITE STATE MACHINES

## Example-4 (contd)



- Obtain State Table, State Equation and design a circuit

Current State $S$	Inputs $T_A$ $T_B$		Next State $S'$
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

 

24/09/21

Sudarshan TSB, PES University

12

12

## FINITE STATE MACHINES

## Example-4 (contd)



## • State Assignment, State Table

Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = S_1 \oplus S_0$$

$$S'_0 = S_1 S_0 T_A + S_1 S_0 T_B$$

24/09/21

Sudarshan TSB, PES University

13

13

## FINITE STATE MACHINES

## Example-4 (contd)



## • Output Table

Current State		Outputs			
$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10

$$L_{A1} = S_1$$

$$L_{A0} = S_1 S_0$$

$$L_{B1} = S_1$$

$$L_{B0} = S_1 S_0$$

24/09/21


Sudarshan TSB, PES University

14

14

## FINITE STATE MACHINES

## Example-4 (contd)

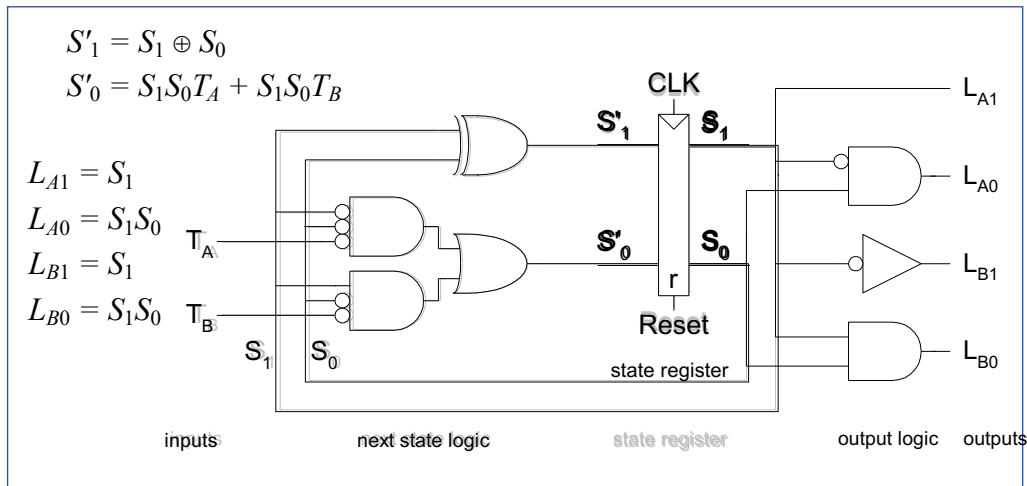

24/09/21

Sudarshan TSB, PES University

15


15

## FINITE STATE MACHINES
 
## Example-5



- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it. The snail smiles whenever the last two digits it has crawled over are 01. Design Moore and Mealy FSMs of the snail's brain.



24/09/21

Sudarshan TSB, PES University

16

16



## FINITE STATE MACHINES


## Example-5 (contd)



## • Moore FSM:

State	Encoding
S0	00
S1	01
S2	10

## Moore FSM

 

Current State		Inputs	Next State	
$S_1$	$S_0$	$A$	$S'_1$	$S'_0$
0	0	0	0	1
0	0	1	0	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0

$$S'_1 = S_0 A$$

$$S'_0 = A'$$

24/09/21

Sudarshan TSB, PES University

17

17


## FINITE STATE MACHINES

## Example-5 (contd)



Current State		Output
$S_1$	$S_0$	$Y$
0	0	0
0	1	0
1	0	1

$$Y = S_1$$

 

24/09/21

Sudarshan TSB, PES University

18

18

## FINITE STATE MACHINES

## Example-5 (contd)





## • Mealy FSM

State	Encoding
S0	00
S1	01

Current State	Input	Next State	Output
$S_0$	$A$	$S'_0$	$Y$
0	0	1	0
0	1	0	0
1	0	1	0
1	1	0	1

## Mealy FSM

  

24/09/21

Sudarshan TSB, PES University

19


19

## FINITE STATE MACHINES

## Example-4 (contd)



## • Moore &amp; Mealy Timing Diagram:

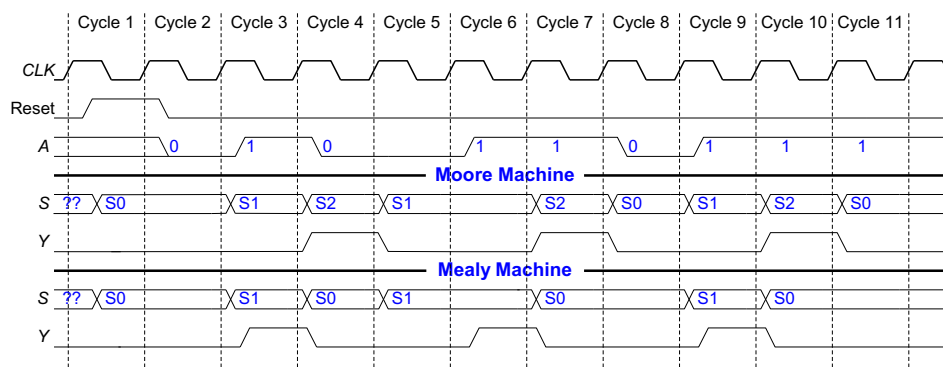

24/09/21

Sudarshan TSB, PES University

20

20



## THANK YOU

---

**Sudarshan T S B. Ph.D.,**  
Department of Computer Science & Engineering  
**sudarshan@pes.edu**  
+91 80 6666 3333 Extn 215

21